

VAVUNIYA CAMPUS OF THE UNIVERSITY OF JAFFNA

First Examination in Information and Communication

Technology - 2015


Second Semester – January / February 2017

ICT 1223 Basic Electronics and Digital Logic Design

Answer Five Questions only

Time: Three hours

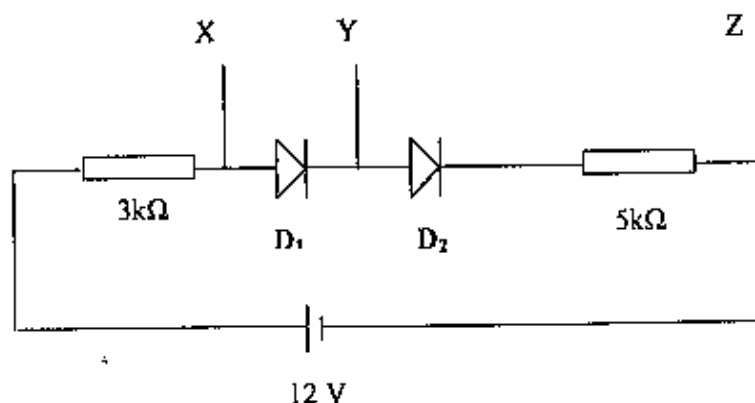- Q1. (a) Explain the difference between conductors, insulators and semiconductors on the basis of energy band? (Marks 20)
- (b) Name three acceptor and three donor materials for doping of a semiconductor. (Marks 20)
- (c) Explain the formation of depletion region and barrier potential of a p-n junction. Hence illustrate Charge density, Electric field strength and Potential variation across the junction. (Marks 40)
- (d) Calculate the conductivity at 300K for Silicon with 10^{24} m^{-3} phosphorus atoms. Mobility of electrons in silicon at 300K is $0.135 \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}$. (Marks 20)
- Q2. (a) Explain the forward and reverse bias characteristic of a p-n junction Diode. (Marks 20)
- (b) Figure shows a series circuit containing resistors of $3\text{k}\Omega$, $5\text{k}\Omega$ and silicon diodes D_1, D_2 . The knee voltage of the silicon diodes is 0.7 V .



Calculate

- (i) the current through the circuit.
- (ii) the voltage between X and Z
- (iii) the voltage between Y and Z

If D_2 is connected in the opposite direction find the followings:

- (i) the voltage between X and Z
- (ii) the voltage between Y and Z


(Marks 50)

- (b) Draw a full – wave bridge rectifier circuit and explain the action of each electronic components briefly. (Marks 30)

- Q3. (a) Zener diode is one of the special diode used in the electronic circuits. Explain how they are usually doped and the size of the depletion region. (Marks 20)

- (b) Sketch and explain the $I - V$ characteristic of a Zener diode. Hence state the use of Zener diode in power supply unit. (Marks 30)

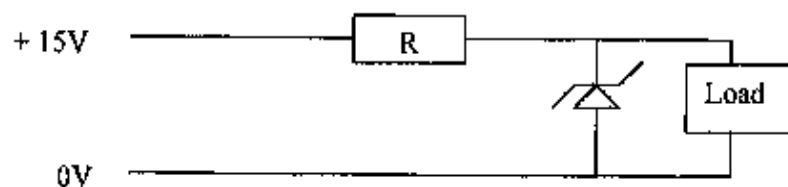- (c) Figure shows a regulated voltage supply circuit. It produces a stabilized output of 6 V from a nominal 15 V supply. The current passing through load is 100mA. The minimum diode current needed to function is 10mA.




- (i) What voltage rating should be chosen for the diode?
- (ii) Calculate the Value of the resistor R.
- (iii) If the Load is removed from the circuit, calculate the power dissipated by the Zener diode.

(Marks 50)


- Q4. (a) Illustrate and explain the three regions and its partial importance in the output characteristics curve of a common emitter configuration. (Marks 25)
- (b) Explain how Transistor can be used as a switch with the help of a circuit diagram. Hence write the advantages of using transistor as switch. (Marks 25)
- (d) Compute the collector current, base current, emitter voltage and collector voltage for the following circuit. ($V_{BE}=0.7\text{ V}$ and dc current gain $\beta = 200$)

(Marks 50)

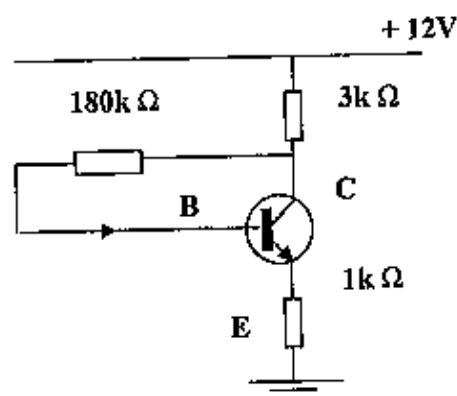

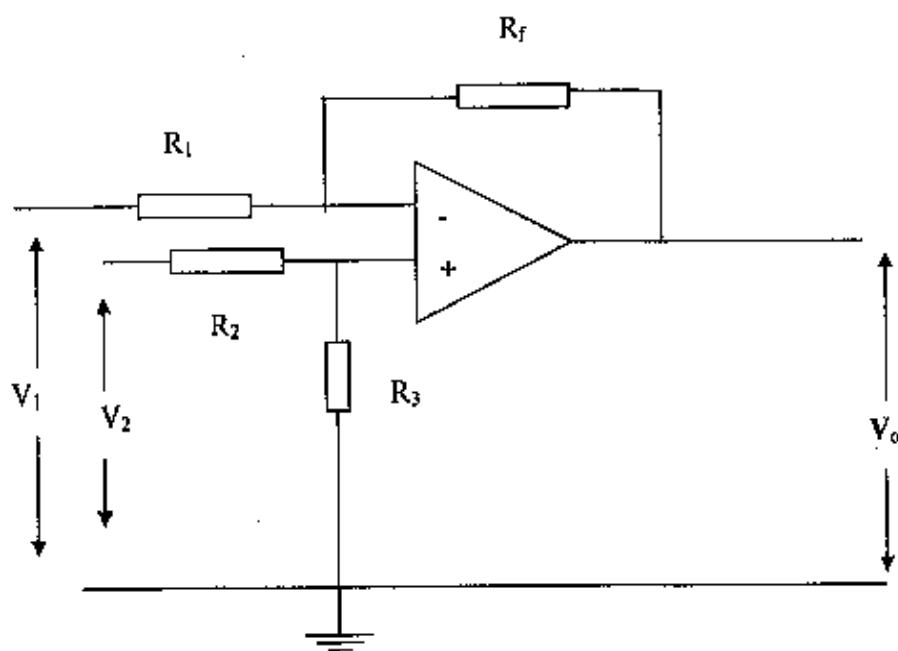- Q5. (a) List the advantages of using integrated circuits (ICs) compared to discrete circuits. (Marks 15)
- (b) Show that the "closed loop gain" A and "open - loop gain" A_o of an operational amplifier can be related as $A = \frac{A_o}{1 + \beta A_o}$ where β is the feedback factor. (Marks 20)
- (c) Write the fundamental properties of operational amplifier. (Marks 15)
- (d) Show that the output V_o of the following Differential Amplifier(refer the figure on the next page) is given by

$$V_o = V_2 \frac{(R_f + R_1) R_3}{(R_3 + R_2) R_1} - V_1 \frac{R_3}{R_1} \quad (\text{ Marks 50 })$$



Q6. (a) A logic gate has the following truth table

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

(i) Name the type of the logic gate.

(ii) Draw and label the symbol for this logic gate. (Marks 30)

(b) A chemical process gives out a warning signal ($W = 1$) when the process operates incorrectly. A logic circuit is used to monitor the process and to determine whether $W = 1$.

Input	Binary Values	Description of plant status
C	1	Chemical rate = 20 litres/ second
	0	Chemical rate < 20 litres/ second
T	1	Temperature = 91°C
	0	Temperature > 91°C
X	1	Concentration > 5M
	0	Concentration = 5M

A warning signal ($W = 1$) will be generated if: either (a) Chemical rate < 20 litres/second or (b) Temperature > 91°C and Concentration > 5M or (c) Chemical rate = 20 litres/second and Temperature > 91°C. Construct a truth table to show all the possible situations when the warning signal could be received. Draw a logic circuit. (Marks 70)

*** END ***