



VAVUNIYA CAMPUS OF THE UNIVERSITY OF JAFFNA

First Examination in Information and Communication

Technology - 2017

Second Semester – March / April 2019


ICT 1223 Basic Electronics and Digital Logic Design

Answer Five Questions only

Time: Three hours

- Q1.** (a) (i) Explain the difference between conductors, insulators and semiconductors on the basis of energy band? [20%]
- (ii) Explain how can the conductivity of a semiconductor be increased? [20%]
- (iii) Intrinsic carrier concentration in a semiconductor is $2.1 \times 10^{13} \text{ cm}^{-3}$. Find the intrinsic resistivity of the semiconductor. The electron and hole mobilities are $\mu_e = 3900 \text{ cm}^2 \text{ V}^{-1} \text{ s}^{-1}$ and $\mu_h = 1900 \text{ cm}^2 \text{ V}^{-1} \text{ s}^{-1}$ respectively. [30%]
- (b) (i) List the advantages of using fiber optic cable compare to copper cable in the communication sector. [15%]
- (ii) Name the major electronic devices needed in fiber optic communication and discuss briefly how the communication is done. [15%]
- Q2.** (a) Explain the formation of depletion region and barrier potential of a p-n junction. [30%]
- (b) Sketch and explain the forward and reverse characteristic of a p-n junction. [20%]

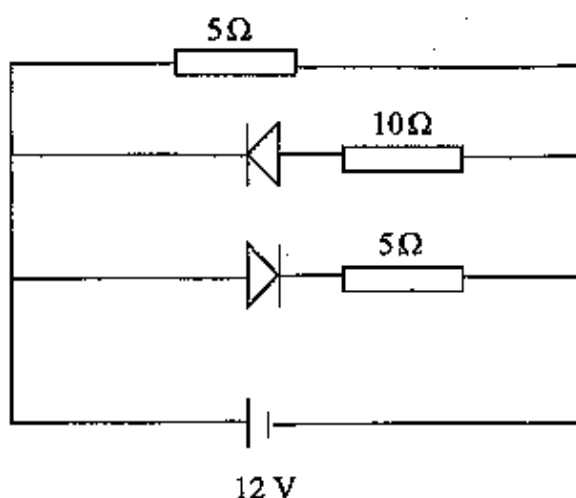
- (c) What currents will flow each of the three branches of the following circuit. The knee voltage of the silicon diodes is 0.7 V. [30%]



- (d) Draw a half-wave rectifier circuit and explain the action briefly. Explain the disadvantages in using half-wave rectifier. [20%]


- Q3. (a) Give three different types of special diodes and explain their applications. [20%]
- (b) Sketch and explain the I - V characteristic of a Zener diode. [20%]
- (c) Compare normal diode and Zener diode in the followings: doping, Size of the depletion region and action when connected in reverse biased. [20%]
- (d) Figure shows a zener diode used to produce a stabilized output of 8 V from a nominal 12 V supply. The zener diode must have a minimum current of 10 mA passing through it to maintain its voltage. The current passing through load is 100 mA. [40%]

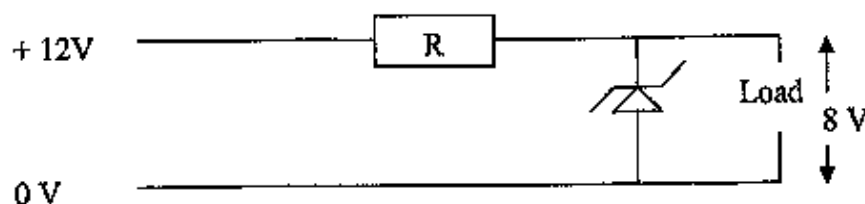- (i) Calculate the ideal value of R , and power dissipated by R under these conditions.




- (ii) If the output current from this power supply falls to zero while the input voltage is still present, calculate the power dissipated by the zener diode.

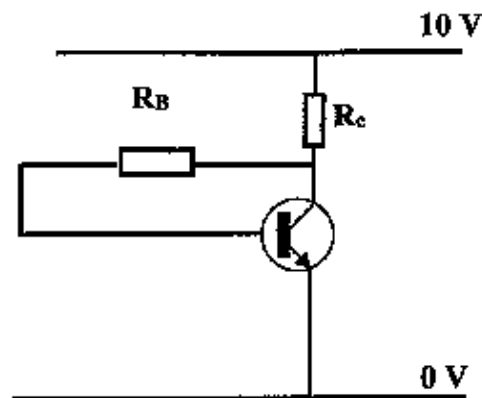- Q4.** (a) Explain the Transfer characteristics of a transistor in common emitter configuration. (Using I_c Vs I_B curve) [20%]
- (b) What do you mean by transistor biasing? Hence explain how transistor should be biased in the following circuits.
- (i) Transistor as an amplifier
- (ii) Transistor as a switch [30%]
- (c) The following figure shows the collector feedback bias circuit for a Silicon npn transistor. If $R_C = 1k\Omega$, $R_B = 500k\Omega$ and $\beta = 50$, find the collector current. [50%]




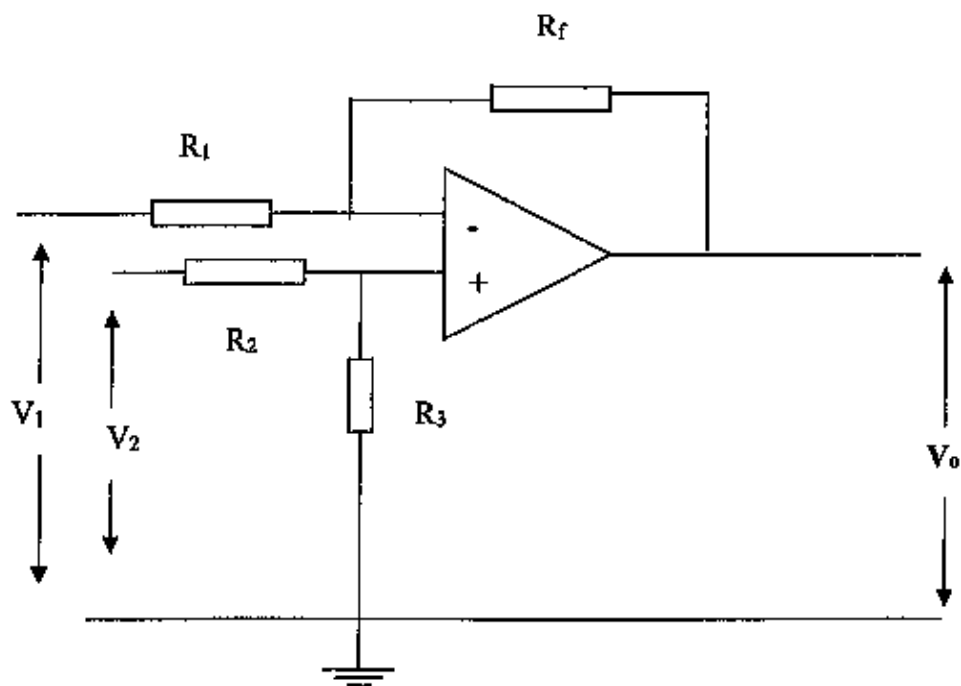- Q5.** (a) List the advantages of using integrated circuits (ICs) compared to discrete circuits. [20%]
- (b) Write the fundamental properties of operational amplifier. [20%]
- (c) Show that the "closed loop gain" A and "open - loop gain" A_o of an operational amplifier can be related as $A = \frac{A_o}{1 + \beta A_o}$ where β is the feedback factor [20%]
- (d) Show that the output V_o of the following Differential Amplifier(refer the figure on the next page) is given by

$$V_o = V_2 \frac{(R_f + R_1) R_3}{(R_3 + R_2) R_1} - V_1 \frac{R_3}{R_1} \quad [40\%]$$



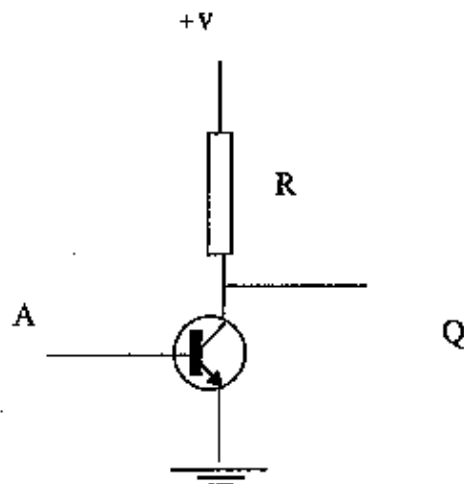- Q6. (a) A logic gate circuit diagram is given bellow. If A is the input and Q is the out put then complete the truth table.



- (i) Name the type of the logic gate.
 - (ii) Draw and label the symbol for this logic gate. [30%]
- (b) A simple audible warning system for a motorcar is activated ($W = 1$) when the engine is running ($E = 1$) and either the oil pressure is too low ($P = 0$) or the alternator is not charging ($C = 0$). To implement this warning system, draw a logic circuit using NOT and NAND gates.

[70%]

*** END ***