



## VAVUNIYA CAMPUS OF THE UNIVERSITY OF JAFFNA

### First Examination in Information and Communication

Technology - 2014


Second Semester – February / March 2016

### ICT 1223 Basic Electronics and Digital Logic Design

Answer Five Questions only

Time: Three hours

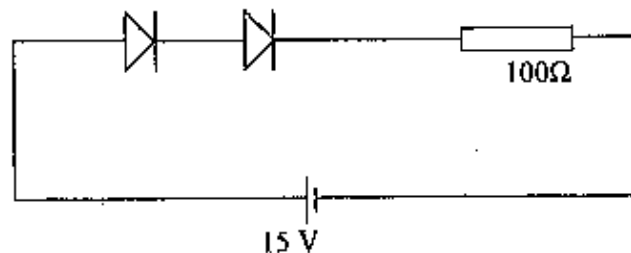- Q1.** (a) (i) Differentiate between intrinsic and extrinsic semiconductors? [25%]  
(ii) Explain the formation of depletion region and barrier potential of a p-n junction. [25%]
- (b) (i) List the advantages of using fiber optic cable compare to copper cable in the communication sector. [25%]  
(ii) Name the major electronic devices needed in fiber optic communication and discuss briefly how the communication is done. [25%]
- Q2.** (a) Sketch and explain the forward and reverse characteristic of a diode. [30%]  
(b) Figure shows a series circuit containing resistor of  $100\Omega$  and two silicon diodes. The knee voltage of the silicon diodes is  $0.7\text{ V}$ .




- (i) Find the current through the circuit.
- (ii) What is the potential drop across the  $100\Omega$  resistor? [30%]

(b) Explain the differences between alternating current and direct current. Hence name three equipments works with direct current. [10%]

(d) Draw a half-wave rectifier circuit and explain the action briefly. Explain the disadvantages in using half-wave rectifier. [30%]

Q3. (a) Explain the characteristic of a Zener diode and its use. [20%]

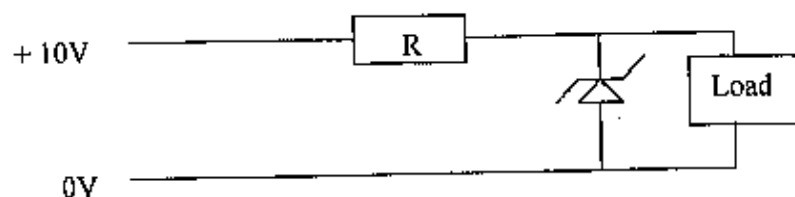(b) Figure shows a regulated voltage supply circuit. It produces a stabilized output of 8 V from a nominal 10 V supply. The current passing through load is 100mA. The current through the diode is 10 mA.




- Name the type of diode used in this circuit.
- In which bias direction is the diode is connected?
- What voltage rating should be chosen for the diode?
- Calculate the ideal value of the resistor R.
- If input voltage rises to 14 V, calculate the current through R at this voltage using the value of R obtain from part (iv) [80%]

Q4. (a) What do you mean by transistor biasing? [20%]


(b) Explain the Transfer characteristics of a transistor in common emitter configuration. ( Using  $I_c$  Vs  $I_B$  curve) [20%]

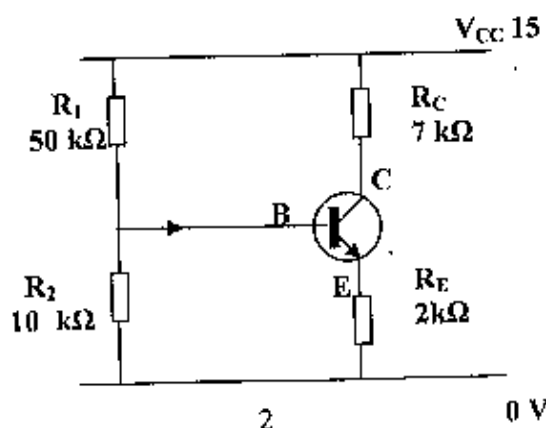(c) Compute the base, emitter and collector voltages for the voltage divider bias


npn transistor circuit shown in the figure. (  $V_{BE}=0.7\text{ V}$  ) [60%]



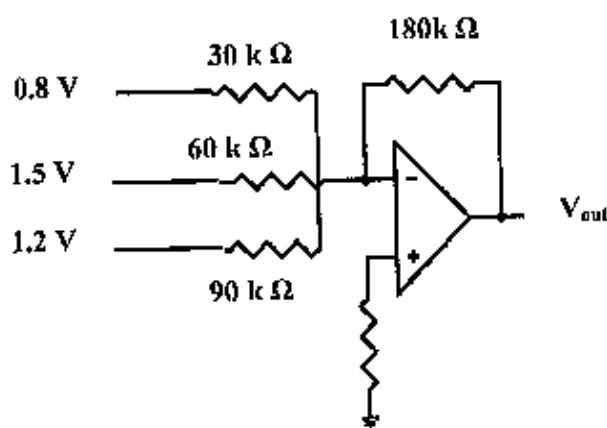- Q5. (a) List the advantages of using integrated circuits (ICs) compared to discrete circuits. [20%]
- (b) What is meant by open-loop gain of an op-amp? [10%]
- (c) What arrangements in an op-amp can control the gain? [10%]
- (d) Illustrate the transfer characteristic of an operational amplifier. [20%]
- (e) Find the output voltage ( $V_o$ ) for the summing op-amp shown in the circuit. [40%]



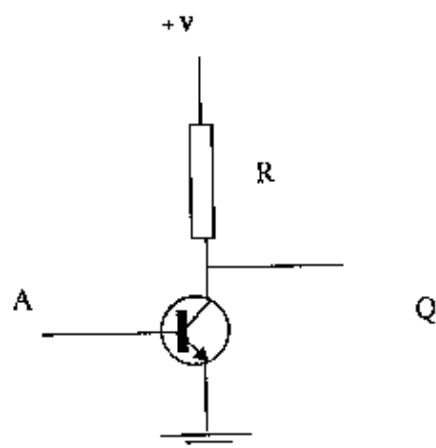- Q6. (a) A logic gate circuit diagram is given below. If A is the input and Q is the output then complete the truth table.



- (i) Name the type of the logic gate.
- (ii) Draw and label the symbol for this logic gate. [30%]
- (b) A simple audible warning system for a motorcar is activated ( $W = 1$ ) when the engine is running ( $E = 1$ ) and either the oil pressure is too low ( $P = 0$ ) or the alternator is not charging ( $C = 0$ ). To implement this warning system, draw a logic circuit using NOT and NAND gates. [70%]

\*\*\* END \*\*\*